

MAHANT BACHITTAR SINGH COLLEGE OF ENGINEERING & TECHNOLOGY, JAMMU

Assignment-1 (Date of Submission 20/09/2016)

SEMESTER: 6TH

COURSE NAME: LIC

COURSE CODE: ECE-504

BRANCH: E&CE / AE&I

- Q2. (a) Draw the Op-amp symbol and explain various Op-amp terminals. List the ideal characteristics of an op-amp. (5)
- (b) What is the difference between compensated and non-compensated op-amps? Explain. (5)
- Q3. (a) Derive an expression for output voltage in case of differential amplifier using two OP-Amps. (5)
- (b) What is an internally compensated op-amp? Draw the frequency response of an op-amp and derive an expression for open loop voltage gain. (5)
- Q4. (a) What is slew rate and its causes? Derive an expression for slew rate. (5)
- (b) For an op-amp having a slew rate of $3 \text{ V} / \mu\text{sec}$. What is the maximum closed loop voltage gain that can be used when the input signal varies by 0.4 V in $12 \mu\text{sec}$? (5)
- (c) For a dual input balanced output, differential amplifier, $V_{CC}=10\text{V}$, $V_{EE}=-10\text{V}$, $R_C=4.7\text{k}\Omega$, $R_E=6.8\text{k}\Omega$ and $R_S=50\Omega$. Determine
- (i) I_{CQ} and V_{CEQ}
 - (ii) The voltage gain
 - (iii) Input and output resistance.
- Assume $h_{fe}=500$, $h_{ie}=18\text{k}\Omega$ and $V_{BE}=0.712\text{V}$. (5)
- Q5. (a) For an op-amp used as an inverting amplifier, the values of R_f and R_i are $47\text{k}\Omega$ and 470Ω respectively. The input offset voltage drift is $28 \mu \text{ V}/^\circ\text{C}$ while input offset current drift is $300 \text{ pA}/^\circ\text{C}$. The amplifier is nulled at 25°C . If the input voltage is 12mV peak sine wave at 2 kHz , then calculate the error voltage and output at 55°C . Also draw the output voltage waveform at 55°C . (5)
- (b) List the four negative feedback configurations. Which two configurations are most commonly used and why? (5)
- Q6. (a) Non-compensated op-amp has a DC gain $A=1,20,000$ and the following break frequencies: $f_{01}=5\text{kHz}$, $f_{02}=320\text{kHz}$, $f_{03}=1\text{MHz}$, and $f_{04}=2\text{MHz}$. Write the open loop gain equation for the op-amp as a function of break frequencies and DC gain A . Also draw the frequency response and phase response curves. (5)
- (b) What is the active load? Where it is used and why. (5)
- (c) Discuss the various methods of realizing high input resistance for an op-amp. Highlight the relative merits and demerits of each. (5)
- (d) Define the common-mode rejection ratio (CMRR) and explain the significance of a relatively large value of CMRR. (5)